

# **Lecture 15**

# **Pipelined Datapath and Control**

**School of Computer Science and Engineering**  
**Soongsil University**

# 4. The Processor

- 4.1 Introduction
- 4.2 Logic Design Conventions
- 4.3 Building a Datapath
- 4.4 A Simple Implementation Scheme
- 4.5 An Overview of Pipelining
- 4.6 **Pipelined Datapath and Control**
- 4.7 Data Hazards: Forwarding versus Stalling
- 4.8 Control Hazards
- 4.9 Exceptions
- 4.10 Parallelism via Instructions
- 4.11 Real Stuff: The ARM Cortex-A8 and Intel Core i7 Pipelines
- 4.12 Going Faster: Instruction-Level Parallelism and Matrix Multiply

# Pipelined Version of the Datapath

## ■ Pipeline register

- ❖ Separation of the two stages
- ❖ Hold information produced in previous cycle

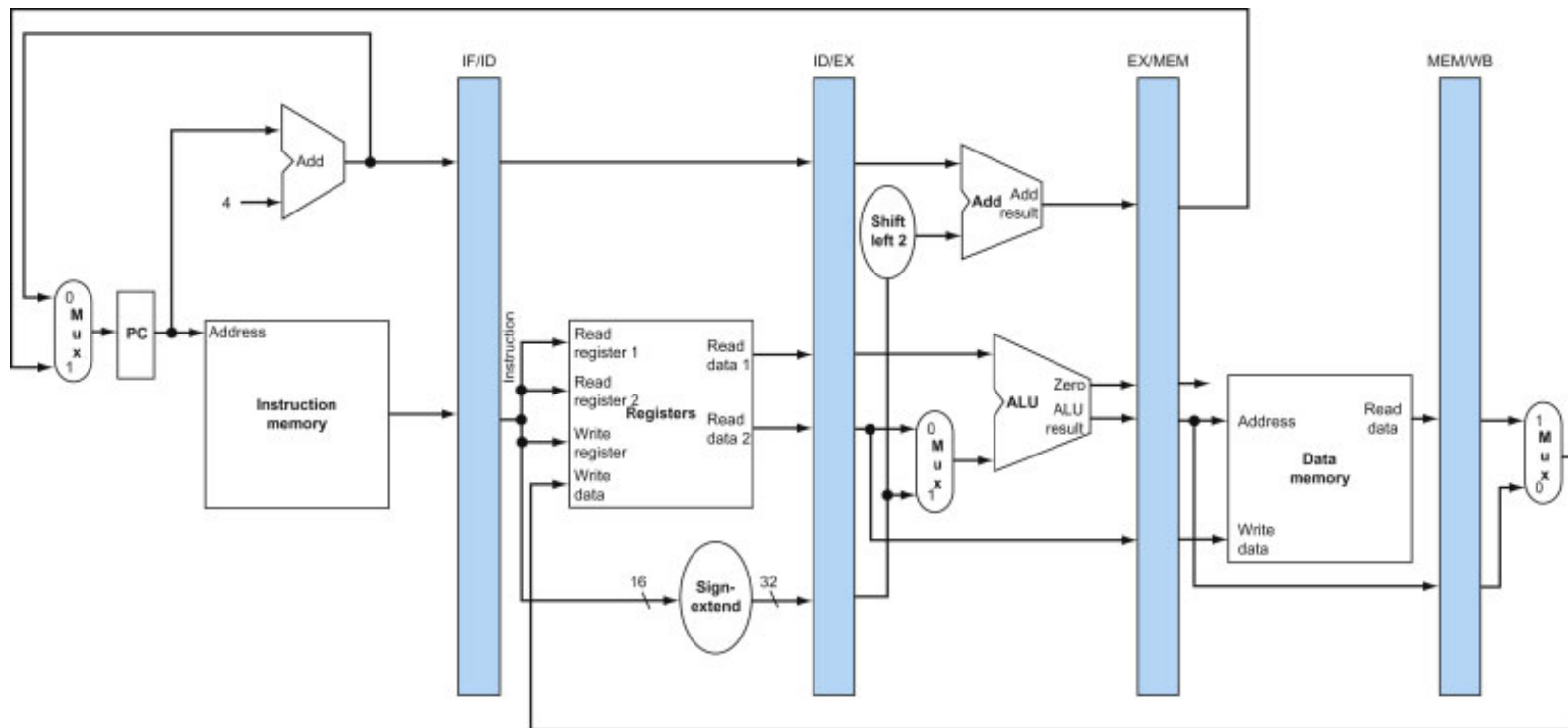


Figure 4.35

# lw Instruction in IF Stage

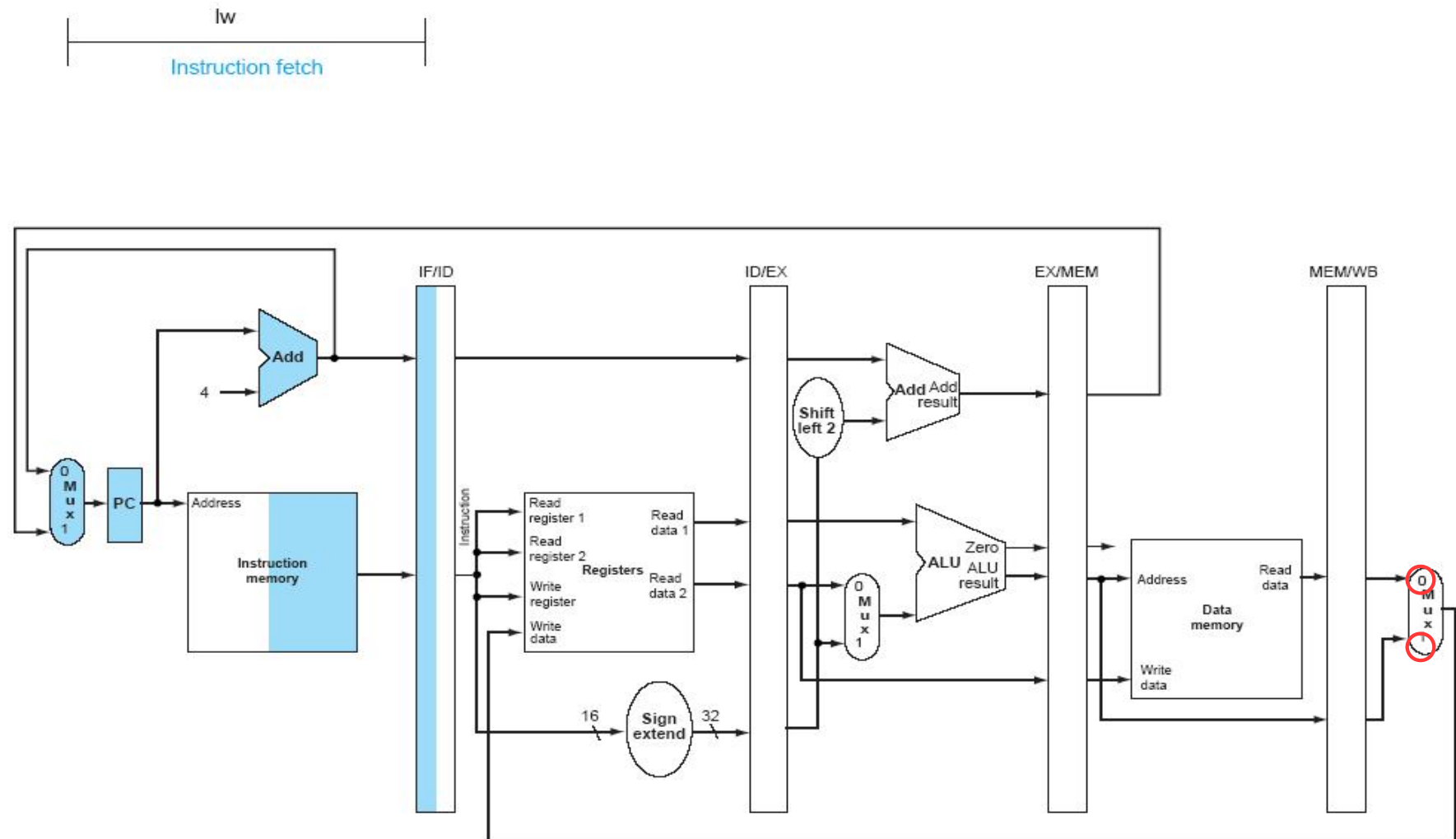


Figure 4.36(a)

# lw Instruction in ID Stage

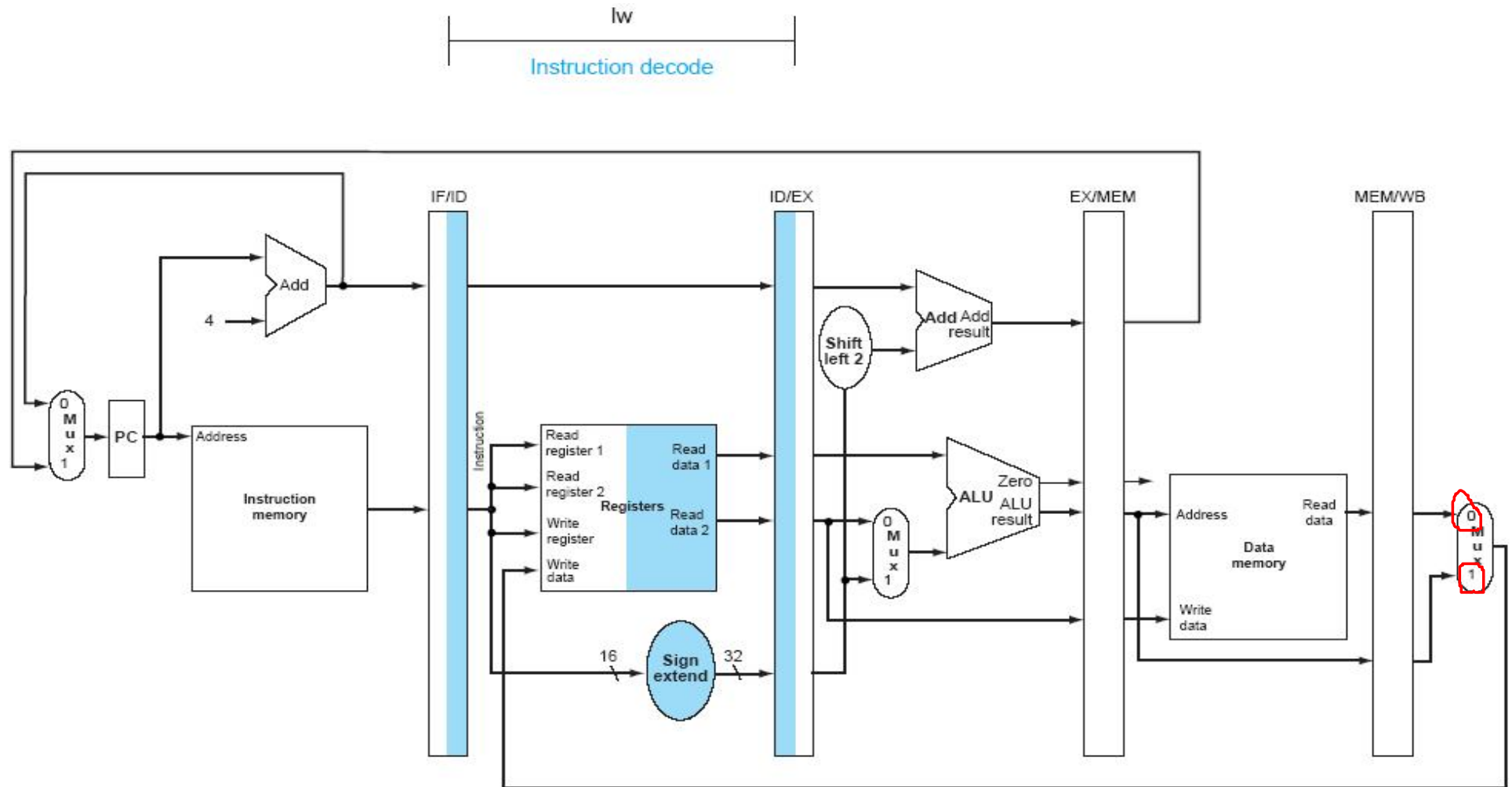


Figure 4.36(b)

# lw Instruction in EX Stage

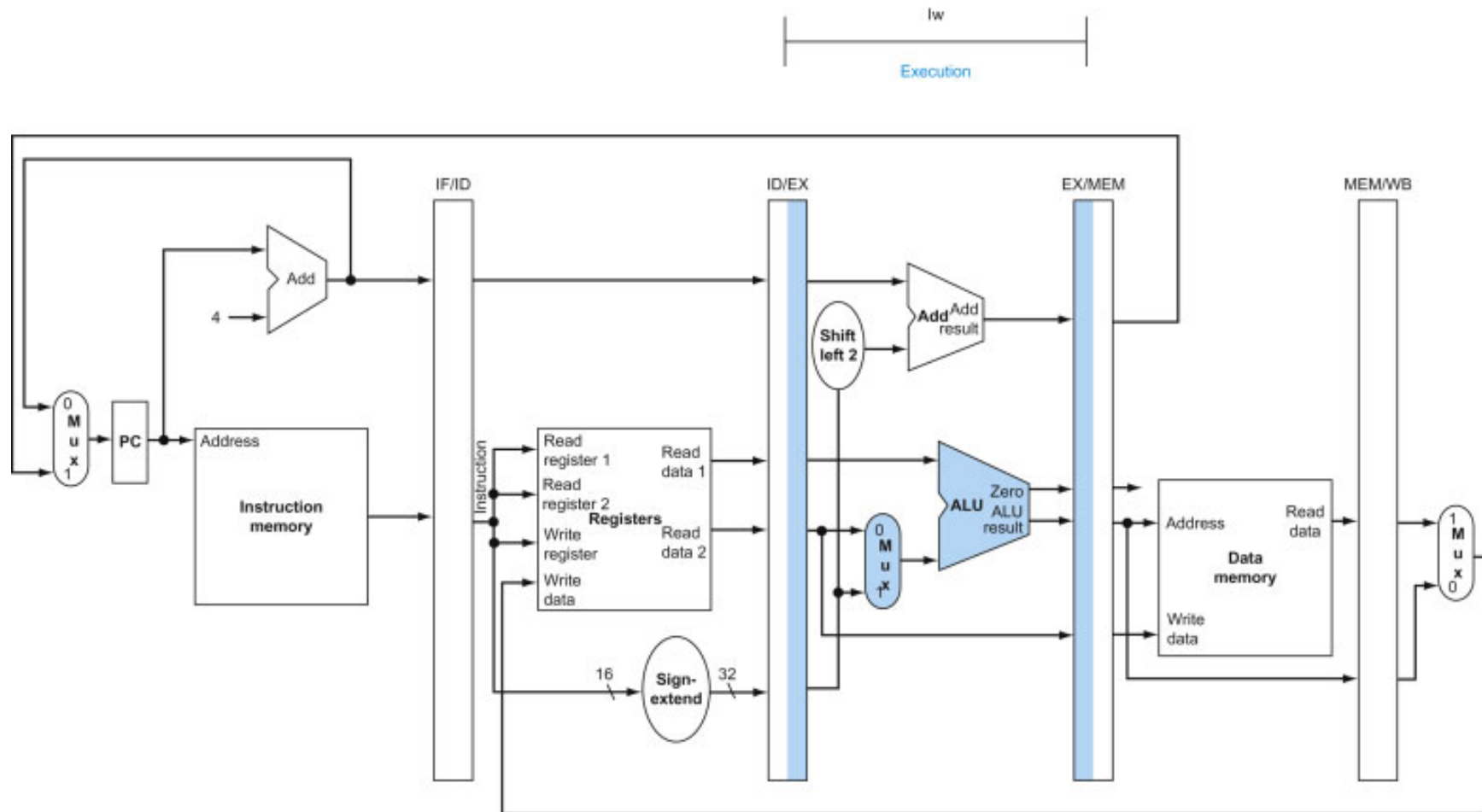


Figure 4.37

# lw Instruction in MEM Stage

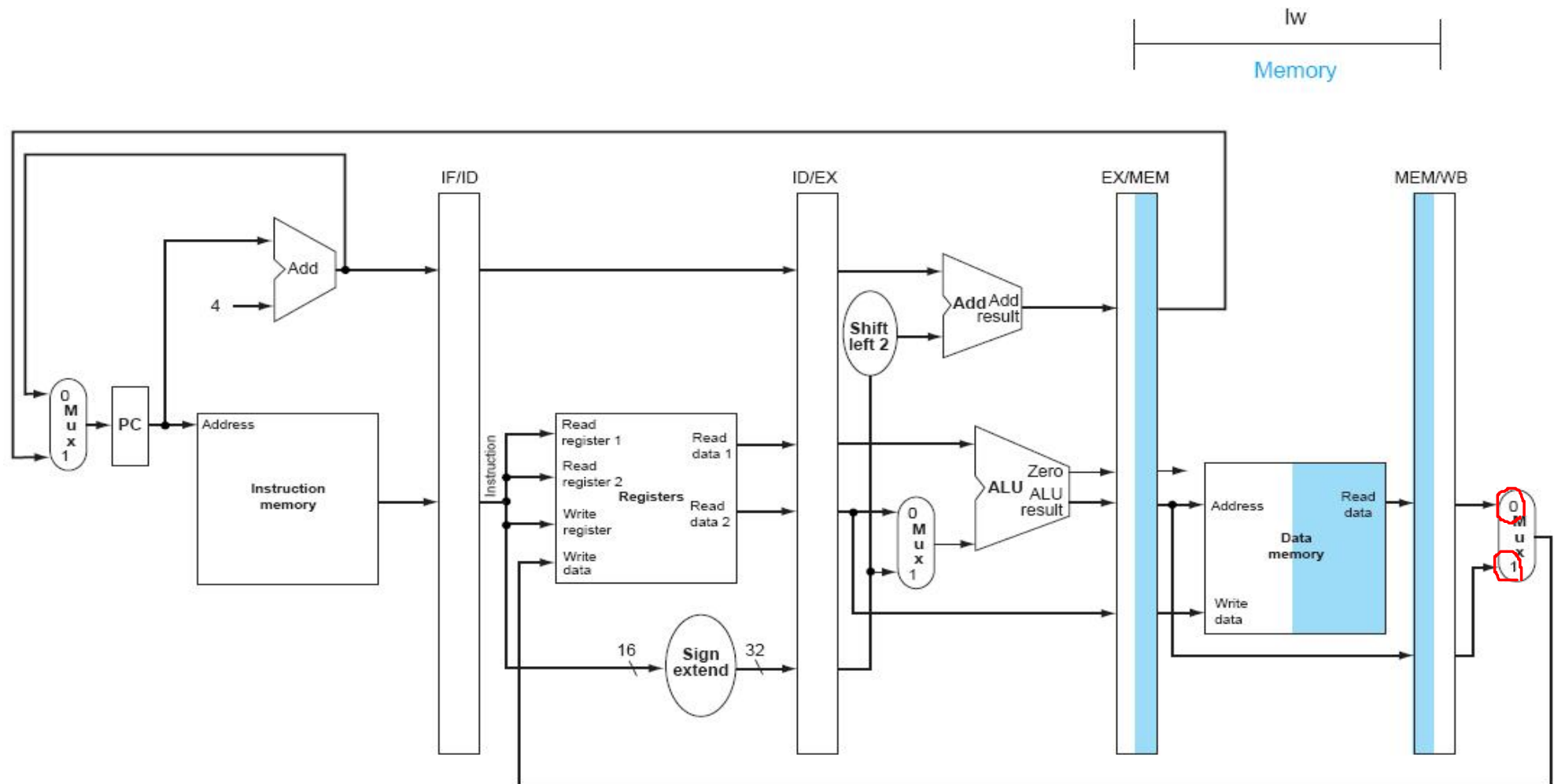


Figure 4.38(a)

# I w Instruction in WB Stage

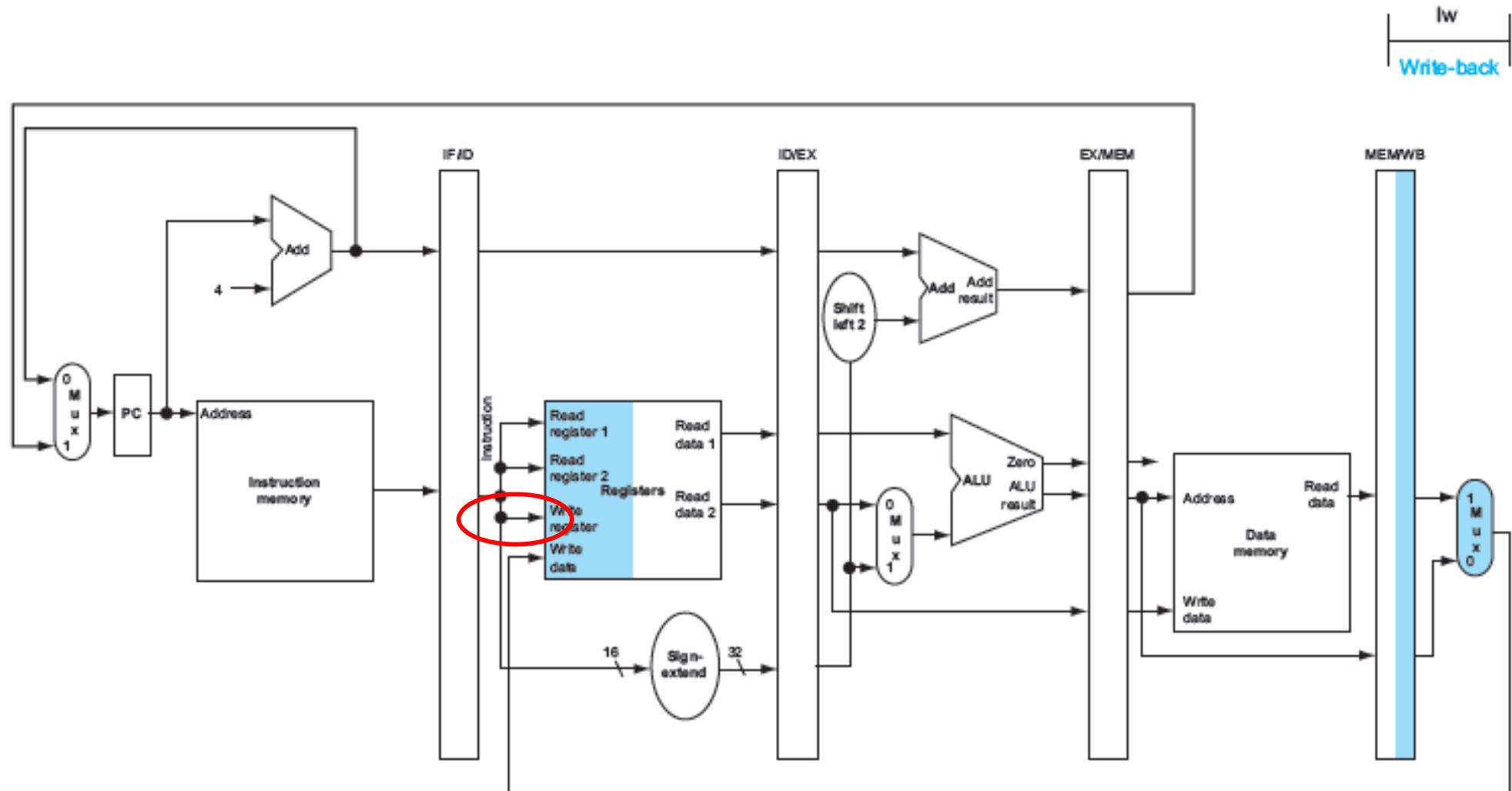


Figure 4.38(b)



# Corrected Pipelined Datapath

## ■ load instruction

- ❖ Write register number: Should be preserved until WB stage

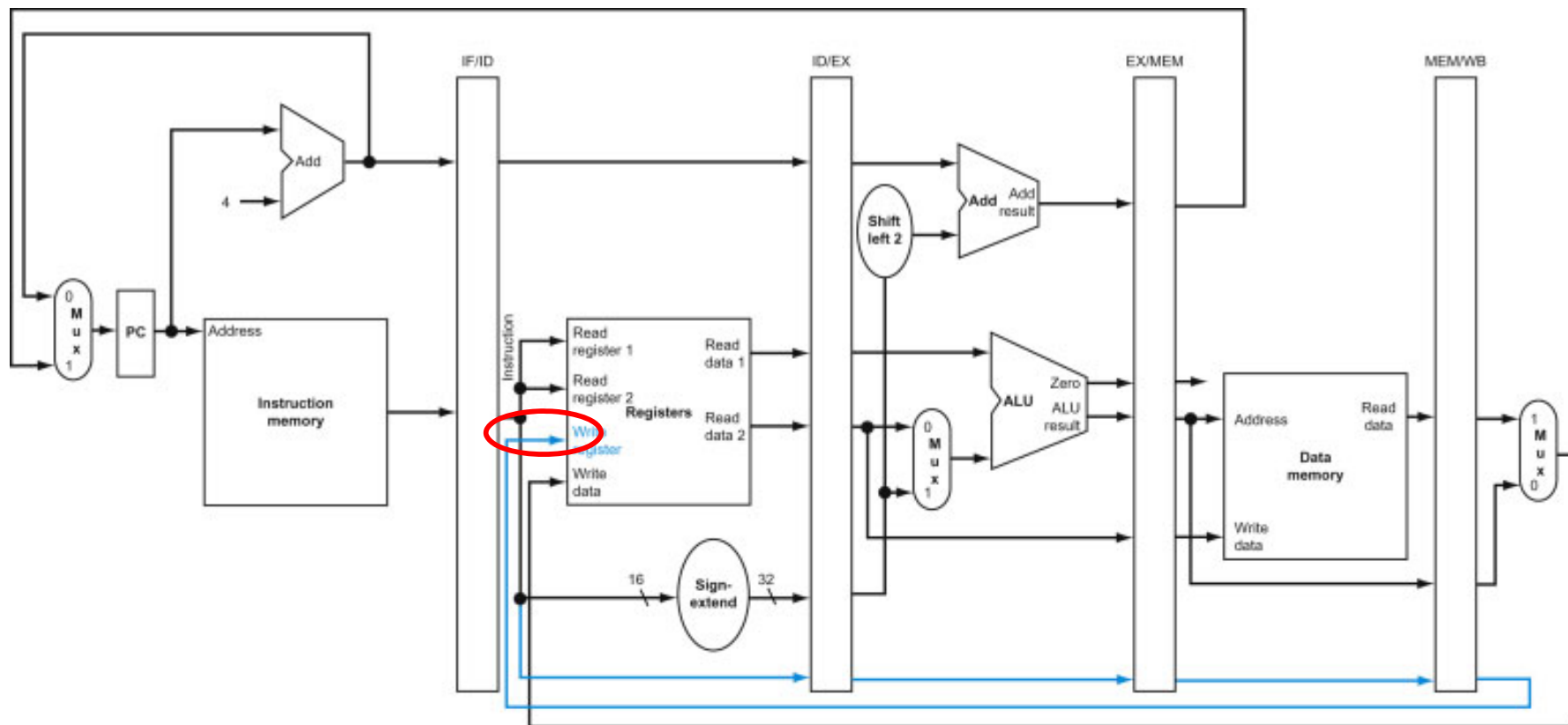


Figure 4.41

# sw Instruction in EX Stage

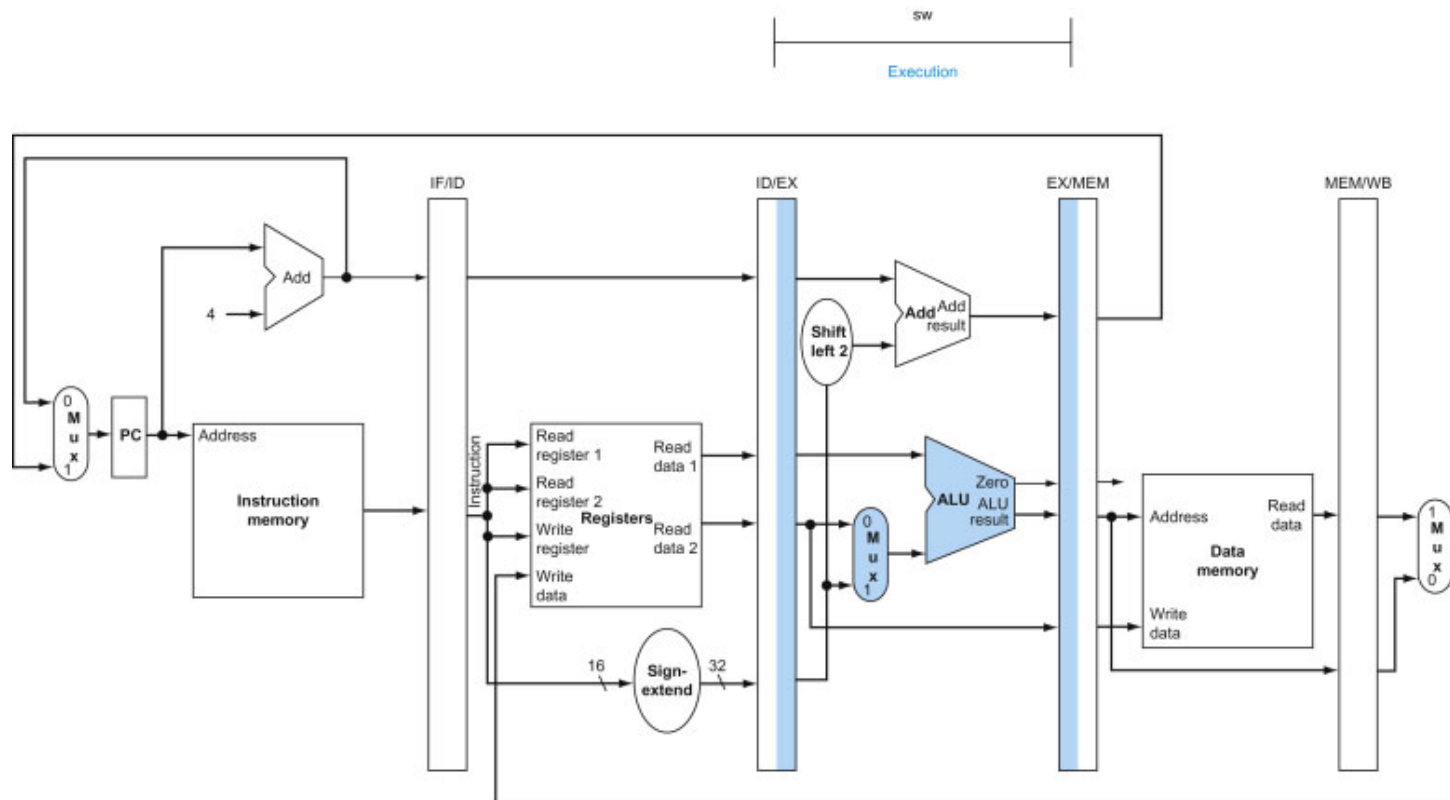


Figure 4.39

# sw Instruction in MEM Stage

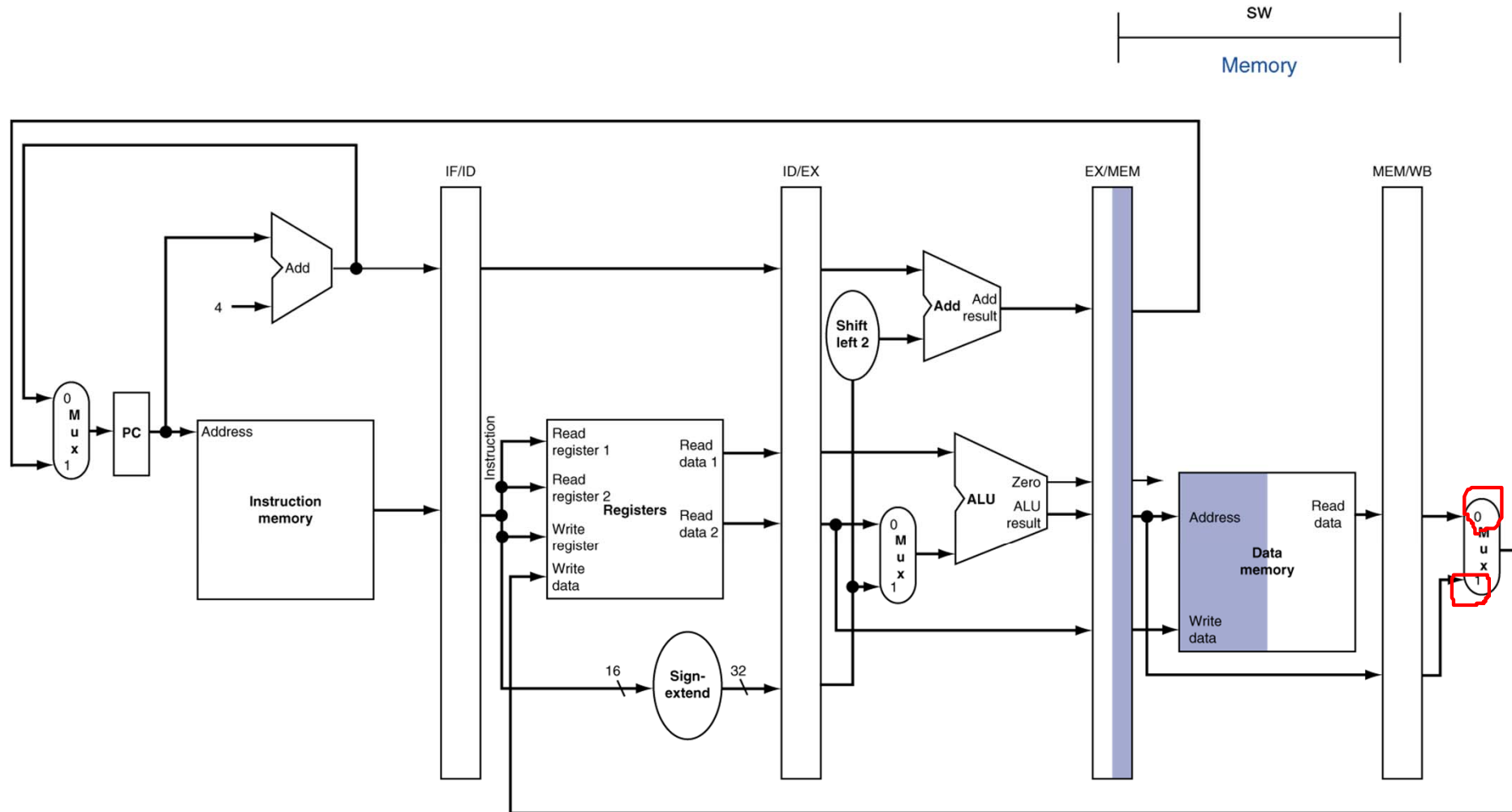


Figure 4.40 (a)

# sw Instruction in WB Stage

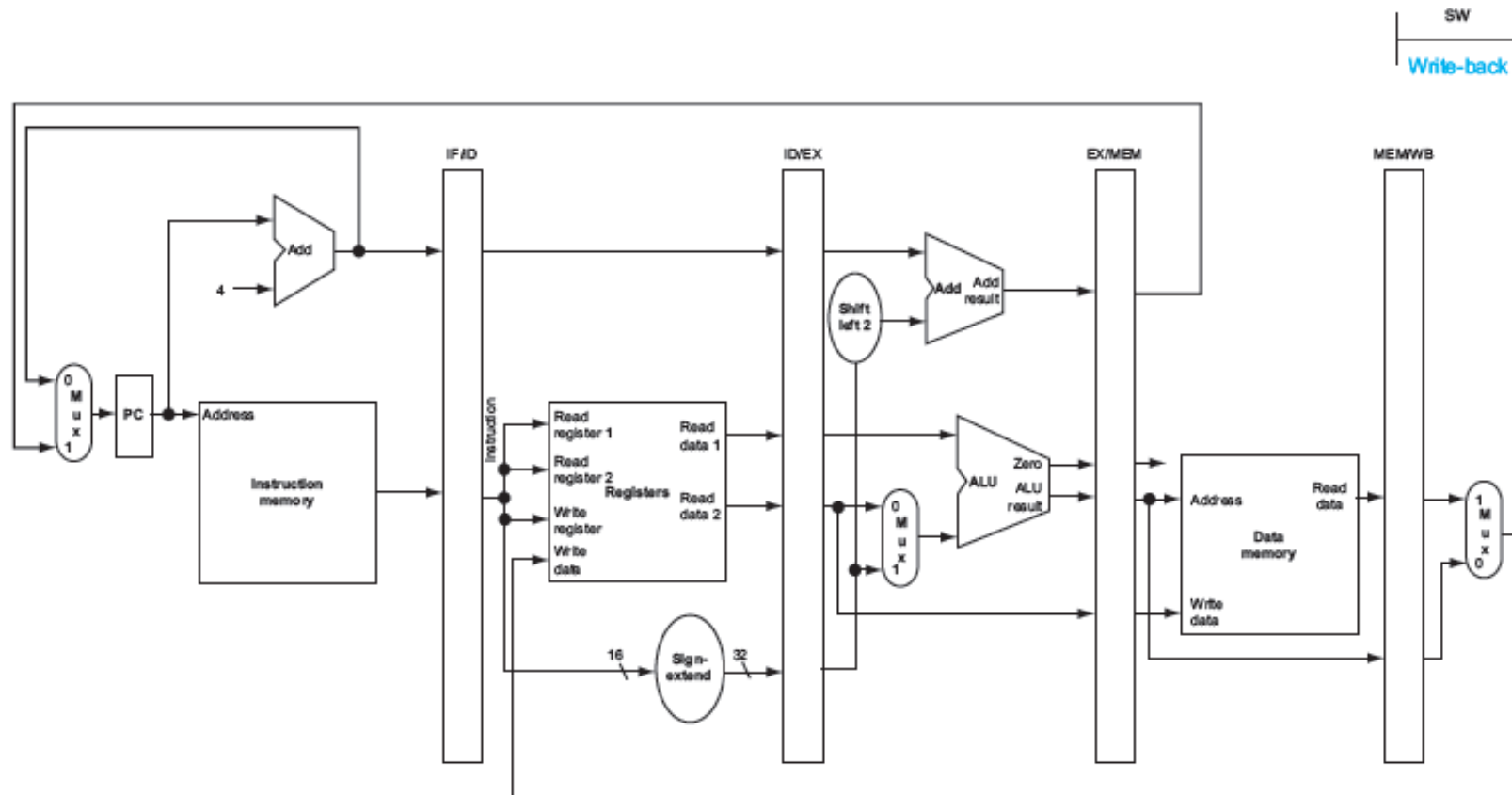


Figure 4.40 (b)

# Pipelined Control

- Pipelined datapath with control signals

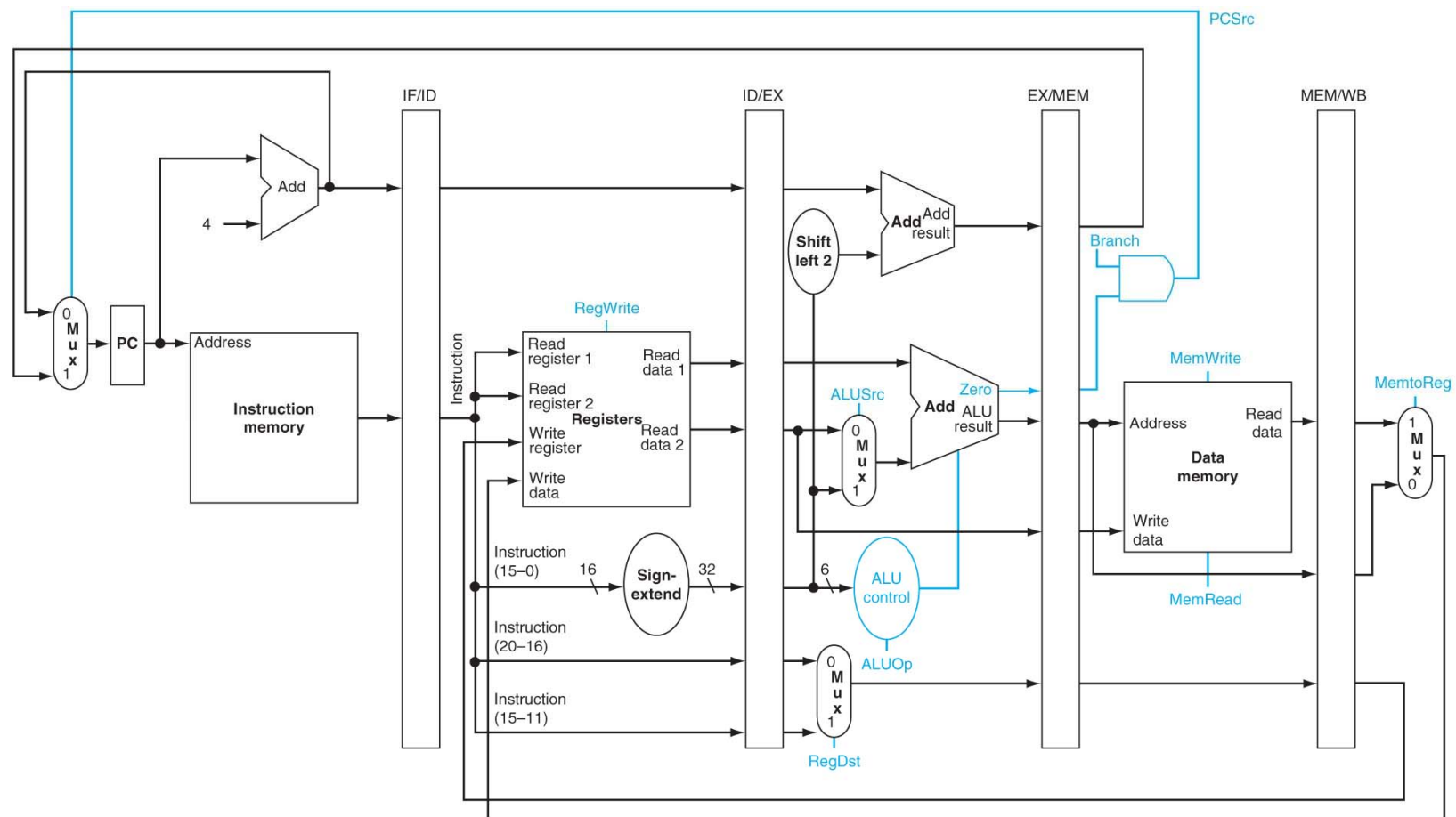


Figure 4.46

# Control Signals

1. IF : nothing ( the same thing happens at every clock cycle)
2. ID : nothing
3. EX : RegDst, ALUOp, ALUSrc
4. MEM : Branch(for beq), MemRead(for lw), MemWrite(for sw)
5. WB : MemtoReg, RegWrite

Instruction	Execution/address calculation stage control lines				Memory access stage control lines			Write-back stage control lines	
	RegDst	ALUOp1	ALUOp0	ALUSrc	Branch	Mem-Read	Mem-Write	Reg-Write	Memto-Reg
R-format	1	1	0	0	0	0	0	1	0
lw	0	0	0	1	0	1	0	1	1
sw	X	0	0	1	0	0	1	0	X
beq	X	0	1	0	1	0	0	0	X

Figure 4.49

# Control Signals for Each Stage

- Control signals derived from instruction

 


Figure 4.50

# Complete Pipelined Datapath

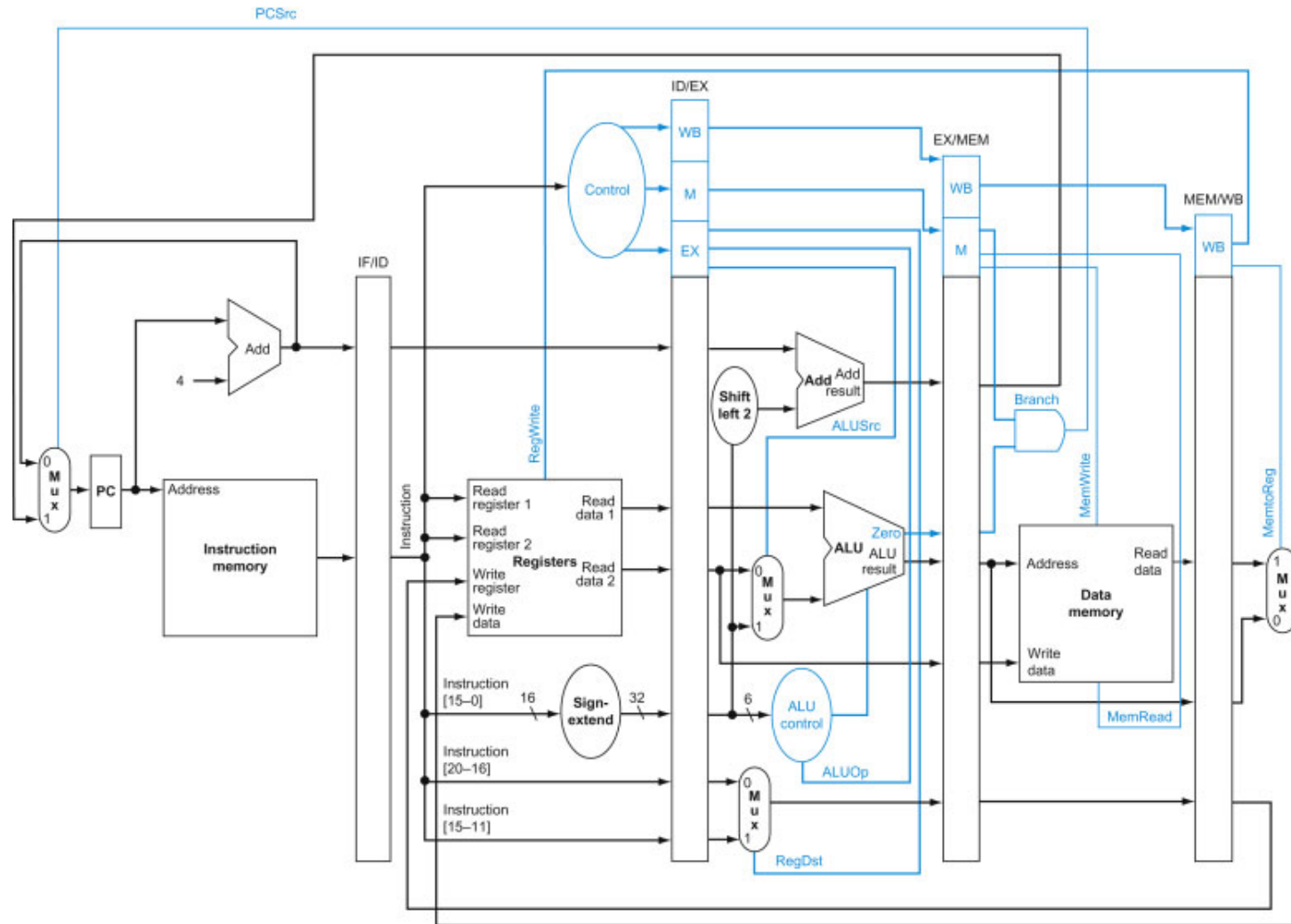


Figure 4.51



# Example: Complete Pipelined Datapath

1000: lw \$1, 81(\$2)  
1004: add \$3,\$4,\$5  
1008: sub \$6,\$7,\$8  
1012: slt \$9,\$10,\$11  
1016: beq \$12,\$13, XX

$\$r = r+1$   
 $M[x] = x*2$

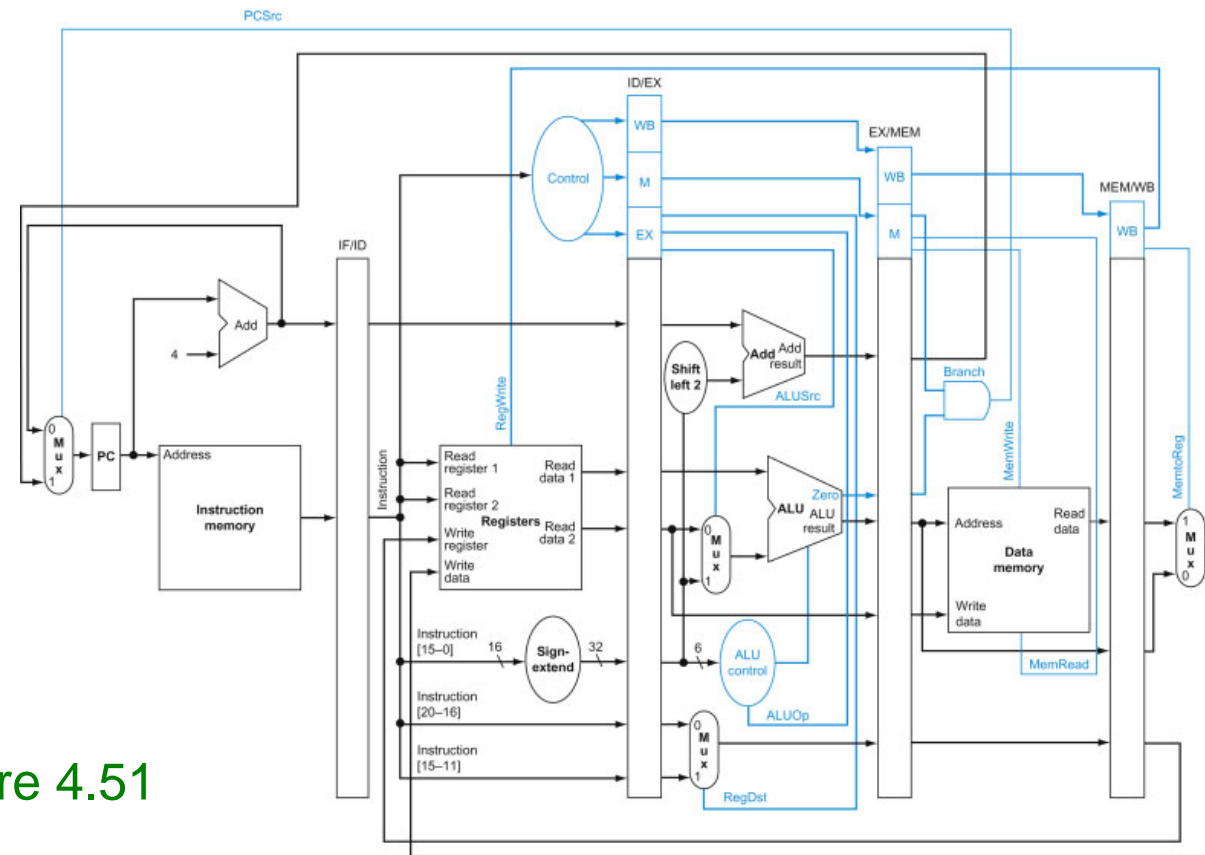


Figure 4.51

# Structural Hazards

- Conflict for use of a resource
- In MIPS pipeline with a single memory
  - ❖ Load/store requires data access
  - ❖ Instruction fetch would have to **stall** for that cycle
    - ◆ Would cause a pipeline “bubble”
- Hence, pipelined datapaths require separate instruction/data memories
  - ❖ Or separate instruction/data caches